 


- Write structural verilog code for 6-bit register.



Code

```
module DFF (D, CLK, Q);
```

```
input D, CLK;
```

```
output reg Q;
```

```
always @ (posedge CLK)
```

```
Q <= D;
```

```
endmodule
```

```
module Shiftreg (D, CLK, Q);
```

```
input D, CLK;
```

```
output [5:0] Q;
```

```
DFF obj1 (D, CLK, Q[5]);
```

```
DFF obj2 (Q[5], CLK, Q[4]);
```

```
DFF obj3 (Q[4], CLK, Q[3]);
```

```
DFF obj4 (Q[3], CLK, Q[2]);
```

```
DFF obj5 (Q[2], CLK, Q[1]);
```

```
DFF obj6 (Q[1], CLK, Q[0]);
```

```
endmodule
```


Testbench

~ timescale 1ns/1ns

~ include "shiftreg.v"

module shiftreg_tb;

reg D, CLK;

wire [5:0] Q;

shiftreg_{dup}(D, CLK, Q);

initial begin

\$dumpfile("shiftreg_tb.vcd");

\$dumpvars(0, shiftreg_tb);

CLK = 0; forever #10 CLK = ~CLK;

end

initial begin

D = 1; #20;

D = 0; #20;

D = 1; #20;

D = 1; #20;

D = 0; #20;


D = 0; #20;

D = 1; #20;

\$display("Test Complete"); → \$finish;

end

endmodule

 Waveform

Q. Write verilog code for an N-bit register.


Code

```
module nbit(D, clk, Q);
    parameter n=4; integer i=0;
    input [n-1:0] D;
    input clk;
    output reg [n-1:0] Q;
    always @ (negedge clk)
        Q <= D;
endmodule
```

Testbench

```
~ timescale 1ns/1ns
~ include "nbit.v"
```

```
module nbit tb;
    reg [3:0] D;
    reg clk;
    wire [3:0] Q;
    nbit obj (D, clk, Q);
    initial begin
        $dumpfile("nbit.tb.vcd");
        $dumpvars(0, nbit_tb);
        clk = 0; forever #10 clk = ~clk;
        end
    initial begin
        D = 4'b 0010; #20;
        D = 4'b 1001; #20;
        D = 4'b 1010; #20;
        D = 4'b 0001; #20;
        $display("Test complete");
        $finish;
    end
endmodule
```

  

Waveform

63
24/10/

3. Design and simulate a shift register with the parallel load that operates ~~reset~~ according to the following function table:

shift	load	Register Operation
0	0	Shift left
0	1	Load parallel data
1	X	No change

Diagram



```

module DFF (D, Clk, Reset, Q);
input D, Clk, Reset;
output reg Q;
always @ (posedge Clk or posedge Reset)
begin
if (Reset)
Q <= 0;
else
Q <= D;
end
endmodule

```



```

module MUX4to1(w,s,f);
input [3:0]w;
input [1:0]s;
output reg f;
always @ (s or w)
begin

```

```

    if (s == 0)
        f = w[0];

```

```

    else if (s == 1)
        f = w[1];

```

```

    else if (s == 2)
        f = w[2];

```

```

    else
        f = w[3];

```

```

end

```

```

endmodule

```

```

~include "DFF.v"

```

```

~include "MUX4to1.v"

```

```

module Pshift(I,Reset,clk,s,A,ser,in);

```

```

input [3:0]I;

```

```

input [1:0]S;

```

```

input Reset, clk, ser, in;

```

```

output [3:0]A;

```

```

wire [3:0]f;

```

```

MUX4to1 mux4 ({A[3], A[3], I[3], A[2]}, s, f[3]);

```

```

MUX4to1 mux3 ({A[2], A[2], I[2], A[1]}, s, f[2]);

```

```

MUX4to1 mux2 ({A[1], A[1], I[1], A[0]}, s, f[1]);

```

```

MUX4to1 mux1 ({A[0], A[0], I[0], ser, in}, s, f[0]);

```

```

DFF dff4 (f[3], clk, Reset, A[3]);

```

```

DFF dff3 (f[2], clk, Reset, A[2]);

```

```

DFF dff2 (f[1], clk, Reset, A[1]);

```

```

DFF dff1 (f[0], clk, Reset, A[0]);

```

```

endmodule

```


Testbench

~ timescale 1ns/1ns

~ include "Pshift.v"

module Pshift_tb;

reg [3:0] I;

reg [1:0] S;

reg Reset, clk, ser_in;

wire [3:0] A;

Pshift obj (I, Reset, clk, S, A, ser_in);

initial begin

\$dumpfile("Pshift_tb.vcd");

\$dumpvars (0, Pshift_tb);

clk = 0; forever #10 clk = ~clk;

end

initial begin

S = 2'b 01; I = 4'b 1010; Reset = 0; #20;

S = 2'b 00; ser_in = 0; #20;

S = 2'b 00; ser_in = 1; #20;

S = 2'b 01; I = 4'b 0001; #20;

S = 2'b 10; #20;

S = \$display("Test complete");

end

endmodule